

Problem Description

You are given a circuit as input, output the truth table for the circuit.

Input Format (Similar as output format for A)

The first line will consist of an integer T , the number of test cases.

T cases follow. For each case:

The first line will consist of two integers M and N separated by a space, the number of logic gates and the number of variables respectively. The gates are numbered from $N+1 \dots N+M$. The output of the gate numbered $N+M$ is the final output of the circuit.

M lines follow. Each line describes each logic gate. Each logic gate has the following format:

The first token will be either "AND", "OR", or "NOT", depending what is the gate.

If the first token is "NOT", it will be followed by a single integer representing the input index.

Otherwise, it will be followed by two integers separated by a space representing the input index.

Input index is an integer i represents the value of x_i (if $1 \leq i \leq N$), or the output of gate i (if $N + 1 \leq i \leq N + M$)

Input index of gate i must be between 1 and $N+i-1$ inclusive.

Output Format (Same as output format for B)

For each case, you have to output in the following format:

There will be 2^N lines.

The first line will consist of the value of the formula given that ($x_1 = 0, x_2 = 0, x_3 = 0, \dots, x_N = 0$).

The second line will consist of the value of the formula given that ($x_1 = 0, x_2 = 0, x_3 = 0, \dots, x_N = 1$).

The third line will consist of the value of the formula given that ($x_1 = 0, x_2 = 0, x_3 = 0, \dots, x_{N-1} = 1, x_N = 0$).

The fourth line will consist of the value of the formula given that ($x_1 = 0, x_2 = 0, x_3 = 0, \dots, x_{N-1} = 1, x_N = 1$).

...

The 2^N th line will consist of the value of the formula given that ($x_1 = 1, x_2 = 1, x_3 = 1, \dots, x_N = 1$).

If the format above is too complicated to understand, see the I/O sample.

Input Sample

```
1
8 4
OR 1 2
NOT 2
OR 2 3
NOT 4
OR 6 3
OR 7 8
AND 5 9
AND 11 10
```

Output Sample

```
0
0
0
0
0
0
0
1
1
1
0
1
1
0
0
1
1
```

Explanation

The circuit is the output sample from problem A. Therefore, the circuit

should have the same truth table as the input sample from problem A (which is also the input sample from problem B).

Constraint

Time Limit: 2s

$1 \leq T \leq 15$

$1 \leq N \leq 15$

$1 \leq M \leq 100$

Score – (26 points)

There is only one test file for this problem.

Note

Java version used is "gcj-java-3.2.2".

C++ version used is "g++ 4.4.7".